

Project2

Verilog

Arithmetic Logic Unit Synopsys

Lin, Shih-Hao

UTD-ID :2021497449

Yang, Wen-Fu

UTD-ID:2021547369

1. Waveform Compare

 


Figure 1 behavioral code waveform

 


Figure 2 mapped code waveform

By figure1. When opcode equal to 000, $\text{input_X} + \text{input_Y} = \text{output_Z}$, delay 100ns.

001, $\text{input_X} - \text{input_Y} = \text{output_Z}$, delay 100ns.

010, $\text{input_X} \& \text{input_Y} = \text{output_Z}$, delay 100ns.

011, $\text{input_X} | \text{input_Y} = \text{output_Z}$, delay 100ns.

100, $\text{input_X} \wedge \text{input_Y} = \text{output_Z}$, delay 100ns.

101, $\text{input_X} \sim \text{input_Y} = \text{output_Z}$, delay 100ns.

110, $\text{input_X} \% \text{input_Y} = \text{output_Z}$, delay 100ns.

111, $\text{input_X} / \text{input_Y} = \text{output_Z}$, delay 100ns.

By figure2. When opcode equal to 000, $\text{input_X} + \text{input_Y} = \text{output_Z}$.

001, $\text{input_X} - \text{input_Y} = \text{output_Z}$.

010, $\text{input_X} \& \text{input_Y} = \text{output_Z}$.

011, $\text{input_X} | \text{input_Y} = \text{output_Z}$.

100, $\text{input_X} \wedge \text{input_Y} = \text{output_Z}$.

101, $\text{input_X} \wedge \sim \text{input_Y} = \text{output_Z}$.


110, $\text{input_X} \% \text{input_Y} = \text{output_Z}$.

111, $\text{input_X} / \text{input_Y} = \text{output_Z}$.

In Mapped code, the inputs didn't pass through the mux (multiplexer), hence the delay did not occur. Beside delay, two designs would be the same function in generally.

2. Design Vision

Schematic View

 

Total Amount of Cells

Report : cell

Design : alu_test_verilog

Version: L-2016.03-SP3

Date : Tue Sep 8 20:46:05 2020

Attributes:

b - black box (unknown)

h - hierarchical

n - noncombinational

r - removable

u - contains unmapped logic

Cell	Reference	Library	Area	Attributes
C7	nand2	library	1.000000	
C10	nand2	library	1.000000	
C14	nand2	library	1.000000	
C23	nand2	library	1.000000	
C33	nand2	library	1.000000	
C36	nand2	library	1.000000	
C277	nand2	library	1.000000	
C278	nand2	library	1.000000	
C279	nand2	library	1.000000	
C280	nand2	library	1.000000	
C281	nand2	library	1.000000	
.				
.				
.				
.				
.				
.				
.				
output_Z_reg[0]	dff	library	7.000000	n
output_Z_reg[1]	dff	library	7.000000	n
output_Z_reg[2]	dff	library	7.000000	n
output_Z_reg[3]	dff	library	7.000000	n
output_Z_reg[4]	dff	library	7.000000	n
output_Z_reg[5]	dff	library	7.000000	n

output_Z_reg[6]	dff	library	7.000000	n
output_Z_reg[7]	dff	library	7.000000	n
output_Z_reg[8]	dff	library	7.000000	n
output_Z_reg[9]	dff	library	7.000000	n
output_Z_reg[10]	dff	library	7.000000	n
output_Z_reg[11]	dff	library	7.000000	n
output_Z_reg[12]	dff	library	7.000000	n
output_Z_reg[13]	dff	library	7.000000	n
output_Z_reg[14]	dff	library	7.000000	n
output_Z_reg[15]	dff	library	7.000000	n
output_Z_reg[16]	dff	library	7.000000	n
output_Z_reg[17]	dff	library	7.000000	n
output_Z_reg[18]	dff	library	7.000000	n
output_Z_reg[19]	dff	library	7.000000	n
output_Z_reg[20]	dff	library	7.000000	n
output_Z_reg[21]	dff	library	7.000000	n
output_Z_reg[22]	dff	library	7.000000	n
output_Z_reg[23]	dff	library	7.000000	n
output_Z_reg[24]	dff	library	7.000000	n
output_Z_reg[25]	dff	library	7.000000	n
output_Z_reg[26]	dff	library	7.000000	n
output_Z_reg[27]	dff	library	7.000000	n
output_Z_reg[28]	dff	library	7.000000	n
output_Z_reg[29]	dff	library	7.000000	n
output_Z_reg[30]	dff	library	7.000000	n
output_Z_reg[31]	dff	library	7.000000	n
output_Z_reg[32]	dff	library	7.000000	n

.
.
.
.

r76/u_div/l_12	inv	library	1.000000	
r76/u_div/l_13	inv	library	1.000000	
r76/u_div/l_14	inv	library	1.000000	
r76/u_div/l_15	inv	library	1.000000	
r76/u_div/l_16	inv	library	1.000000	
r76/u_div/l_17	inv	library	1.000000	
r76/u_div/l_18	inv	library	1.000000	
r76/u_div/l_19	inv	library	1.000000	
r76/u_div/l_20	inv	library	1.000000	
r76/u_div/l_21	inv	library	1.000000	

r76/u_div/l_22	inv	library	1.000000
r76/u_div/l_23	inv	library	1.000000
r76/u_div/l_24	inv	library	1.000000
r76/u_div/l_25	inv	library	1.000000
r76/u_div/l_26	inv	library	1.000000
r76/u_div/l_27	inv	library	1.000000
r76/u_div/l_28	inv	library	1.000000
r76/u_div/l_29	inv	library	1.000000
r76/u_div/l_30	inv	library	1.000000

Total **4048** cells

7146.000000

3.Design Code

1)ALU

```
module alu_test_verilog( input_X, input_Y, opcode, clock, reset, output_Z);
```

```
    parameter Data_width=32;//building system as 32bits;
```

```
    input [Data_width-1:0] input_X,input_Y;    // define two input;
```

```
    input    clock; //define clock;
```

```
    input    reset;                //define reset;
```

```
    input [2:0] opcode;            //define operation code;
```

```
    output reg [Data_width:0] output_Z;
```

```
reg [Data_width:0] mux ; //multiplexer;
```

```
//designing ALU
```

```
always@( input_X, input_Y, opcode, clock, reset)
begin
  case (opcode)

    3'b000 : mux <= input_X + input_Y; //plus;
    3'b001 : mux <= input_X - input_Y; //minus;
    3'b010 : mux <= input_X & input_Y; //and;
    3'b011 : mux <= input_X | input_Y; //or;
    3'b100 : mux <= input_X ^ input_Y; //XOR;
    3'b101 : mux <= input_X ^~ input_Y; //XNOR;
    3'b110 : mux <= input_X % input_Y; //modules;
    3'b111 : mux <= input_X / input_Y; //divide;

  endcase
end

always@(posedge clock)

  if (reset) begin
```



```
        output_Z=0;
    end
```

```
    else begin
        output_Z =mux;

    end
```

```
endmodule
```

2) testbench

```
module alu_test_verilog_tb;
```

```
    reg [31:0] input_X;//desiding inputs as 32 bits;
    reg [31:0] input_Y;
    reg [2:0] opcode;
    reg clock;
    reg reset;
```

```
    wire [31:0] output_Z;
    wire [31:0] mux;
```

```
alu_test_verilog object(  
    .input_X (input_X),  
    .input_Y (input_Y),  
    .opcode (opcode),  
    .clock (clock),  
    .reset (reset),  
    .output_Z (output_Z)  
);
```

```
initial begin
```

```
input_X = 32'b11110101001101011000011111001010;//Input data;
```

```
input_Y = 32'b11110101101001011000010110101101;//Input data;
```

```
    reset = 1;
```

```
    #100 reset = 0;
```

```
    #100 opcode = 3'b000; //plus;
```

```
    #100 opcode = 3'b001; //minus;
```

```
    #100 opcode = 3'b010; //bit-wise AND
```

```
    #100 opcode = 3'b011; //bit-wise OR
```

```
#100 opcode = 3'b100; //bit-wise XOR;
```

```
#100 opcode = 3'b101; //bit-wise XNOR;
```

```
#100 opcode = 3'b110; //remainder
```

```
#100 opcode = 3'b111; //divide;
```

```
end
```

```
//set the cclock
```

```
initial begin
```

```
    #50 clock = 0;
```

```
end
```

```
always begin
```

```
    #50 clock = 0;
```

```
    #50 clock = 1;
```

```
end
```

```
endmodule
```

3) Synopsys code

```
////////////////////////////////////
```

```
// Created by: Synopsys DC Expert(TM) in wire load mode
```

```
// Version : L-2016.03-SP3
```

```
// Date : Tue Sep 8 21:46:26 2020
```

```
////////////////////////////////////
```

```
module alu_test_verilog ( input_X, input_Y, opcode, clock, reset, output_Z );
```

```
    input [31:0] input_X;
```

```
    input [31:0] input_Y;
```

```
    input [2:0] opcode;
```

```
    output [32:0] output_Z;
```

```
    input clock, reset;
```

```
    wire N76, N77, N79, N80, N81, N82, N84, N85, N86, N87, N88, N89, N90, N91,
```

```
        N92, N93, N94, N95, N130, N131, N132, N133, N134, N135, N136, N137,
```

```
        N138, N139, N140, N141, N142, N143, N144, N145, N146, N147, N148,
```

```
        N149, N150, N151, N152, N153, N154, N155, N156, N157, N158, N159,
```

```
        N160, N161, N162, N163, N164, N165, N166, N167, N168, N169, N170,
```

```
        N171, N172, N173, N174, N175, N176, N177, N178, N179, N180, N181,
```

```
    .
```

```
    .
```

```
    .
```

```
    .
```

```
    .
```

```
    .
```

```
    inv U3846 ( .in(n3711), .out(N294) );
```

```
    inv U3847 ( .in(n3712), .out(N293) );
```

```
inv U3848 ( .in(n3713), .out(N292) );  
inv U3849 ( .in(n3714), .out(N291) );  
endmodule
```